

UNIT NO: 5 SINGLE PHASE AC CIRCUIT (PART A)

1. The power factor at resonance in R-L-C series circuit is

- a. Zero
- b. 0.08 lagging
- c. 0.8 leading
- d. Unity

Answer: d

2. In a R-L-C circuit

- a. Power is consumed in resistance and is equal to IR
- b. Exchange of power takes place between inductor and supply line
- c. Exchange of power takes place between capacitor and supply line
- d. All above are correct

Answer: d

3. In an AC. circuit, a low value of kVAR compared with kW indicates

- a. Low efficiency
- b. High power factor
- c. Unity power factor
- d. Maximum load current

Answer: b

4. The power factor of a D.C. circuit is always

- a. Less than unity
- b. Unity
- c. Greater than unity
- d. Zero

Answer: b

5. Which triangles are used in series ac circuit?

- a. Voltage triangle
- b. Impedance triangle
- c. power triangle
- d. all of the above

Answer: d

6. The product of apparent power and cosine of the phase angle between circuit voltage and current is

- a. True power
- b. Reactive power
- c. Volt-amperes
- d. Instantaneous power

Answer: a

7. In a series resonant circuit, the impedance of the circuit is

- a. Minimum
- b. Maximum
- c. Zero

d. None of the above

Answer: a

8. In a circuit containing R, L and C, power loss can take place in

- a. C only
- b. L only
- c. R only
- d. All above

Answer: c

9. Which of the following refers to a parallel circuit?

- a. The current through each element is same
- b. The voltage across element is in proportion to it's resistance value
- c. The equivalent resistance is greater than any one of the resistors
- d. The current through any one element is less than the source current

Answer: d

10. A sine wave has a frequency of 50 Hz. Its angular frequency is _____ radian/second.

- a. 100π
- b. 50π
- c. 25π
- d. 5π

Answer: a

11. The apparent power drawn by an A.C. circuit is 10 kVA and active power is 8 kW. The reactive power in the circuit is

- a. 4 kVAR
- b. 6 kVAR
- c. 8 kVAR
- d. 16 kVAR

Answer: b

12. The net power in a series R-C circuit is

- a. Zero
- b. Positive
- c. Negative
- d. None of these

Answer: b

13. The two alternating quantities could be added by constructing

- a. Squares
- b. Parallelograms
- c. Rhombus
- d. Trapeziums

Answer: b

14. The power factor of a series RL ac circuit is given by

- a. X_L/R
- b. R/X_L
- c. R/Z
- d. Z/R

Answer: c

15. The low power factor of an ac circuit means that

- a. it causes less voltage drop in the line
- b. it draws more active power
- c. it draws less line current
- d. it draws more reactive power

Answer: d

16. The impedance of circuit is given by $15.5\angle-30^\circ \Omega$. It means that the circuit is

- a. capacitive
- b. inductive
- c. purely resistive
- d. none of the above

Answer: c

17. In RLC series circuit, the inductive reactance is 10Ω and capacitive reactance is 15Ω . The total reactance of the circuit is

- a. 25Ω
- b. 18.03Ω
- c. 5Ω
- d. 1.5Ω

Answer: c

18. In series RL circuit, $R = 5 \Omega$, $X_L = 10 \Omega$ and $X_C = 15 \Omega$. If this circuit is connected to a voltage source $v = 100 \sin(314t + 30^\circ) \text{ V}$, the rms value of the current will be

- a. 14.14 A
- b. 10 A
- c. 5 A
- d. 3.33 A

Answer : b

19. An alternating voltage of $80+j60 \text{ V}$ is applied to a circuit and the current flowing is $4-j2 \text{ A}$. Find impedance of circuit.

- a. 22.37Ω
- b. 23.27Ω
- c. 21.88Ω
- d. 27.22Ω

Answer: a

20. An alternating voltage of $80+j60 \text{ V}$ is applied to a circuit and the current flowing is $4-j2 \text{ A}$. Find power factor of circuit.

- a. 0.5 lag

- b. 0.447 lead
- c. 0.447 lag
- d. none of the above

Answer: c

21. The voltage applied to a circuit is $e = 100 \sin(\omega t + 30)$ and the current flowing in the circuit is $i = 15 \sin(\omega t + 60)$. Determine impedance of the circuit.

- a. 6.67 Ω
- b. 5.57 Ω
- c. 7.67 Ω
- d. 1.67 Ω

Answer: a

22. The voltage applied to a circuit is $e = 100 \sin(\omega t + 30)$ and the current flowing in the circuit is $i = 15 \sin(\omega t + 60)$. Determine resistance of the circuit.

- a. 6.67 Ω
- b. 5.77 Ω
- c. 7.67 Ω
- d. 1.67 Ω

Answer: b

23. A resistor of 20 Ω , inductor of 0.005 H and capacitor of 50 μF are connected in series. A supply voltage 230 V, 50 Hz is connected across the series combination. Calculate inductive reactance.

- a. 16.67 Ω
- b. 15.71 Ω
- c. 17.67 Ω
- d. 14.67 Ω

Answer: b

24. A resistor of 20 Ω , inductor of 0.005 H and capacitor of 50 μF are connected in series. A supply voltage 230 V, 50 Hz is connected across the series combination. Calculate capacitive reactance.

- a. 53.67 Ω
- b. 55.71 Ω
- c. 63.67 Ω
- d. 57.67 Ω

Answer : c

25. Two impedances $Z_1 = 40 \angle 30$ and $Z_2 = 30 \angle 60$ are connected in series across a single phase 230 V, 50 Hz supply. Calculate the current drawn

- a. 4.3 A
- b. 2.3 A
- c. 3.4 A
- d. 5.0 A

Answer: c

26. A coil having a impedance of $50.39 \angle 7.16$ is connected in parallel with capacitor having impedance of $127.32 \angle -90$. If supply voltage is 200 V, single phase, 50 Hz. Calculate current in the coil.

- a. $4.47 \angle 7.16$ A
- b. $5.57 \angle 8.16$ A

- c. $4.97\angle 90$ A
- d. $3.97\angle -7.16$ A

Answer: d

26. A coil having a impedance of $50.39\angle 7.16$ is connected in parallel with capacitor having impedance of $127.32\angle -90$. If supply voltage is 200 V, single phase, 50 Hz. Calculate current in the capacitor.

- a. $4.47\angle 90$ A
- b. $5.57\angle 8.17$ A
- c. $4.97\angle 90$ A
- d. $1.57\angle 90$ A

Answer: d

27. An impedance of $(7+j5) \Omega$ is connected in parallel with another impedance of $(10-j8) \Omega$ across a 230 V, 50 Hz supply. Calculate admittance of the circuit.

- a. $0.16\angle -7.04$ mho
- b. $0.16\angle 7.04$ mho
- c. $-0.16\angle 7.04$ mho
- d. none of the above

Answer: b

28. Resonance occurs in series RLC circuit if following condition is satisfied.

- a. $X_L > X_C$
- b. $X_L < X_C$
- c. $X_L = X_C$
- d. $X_L \neq X_C$

Answer: c

29. Current of circuit at resonance is

- a. Maximum
- b. Minimum
- c. Unity
- d. zero

Answer: a

30. A series RLC circuit has following parameter values: $R = 10 \Omega$, $L = 0.01$ H and $C = 100 \mu\text{F}$. Calculate resonant frequency.

- a. 159.15 Hz
- b. 169.15 Hz
- a. 179.15 Hz
- a. 150.15 Hz

Answer: a